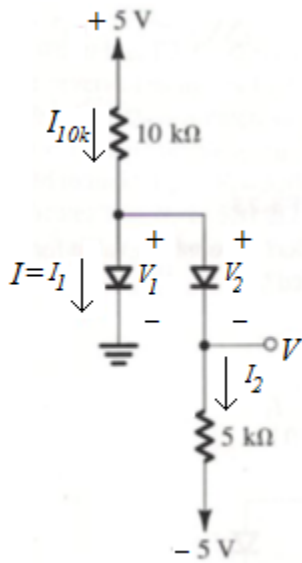


3.9 Assuming that the diodes in the circuits of Fig. P3.9 are ideal, find the values of the labeled voltages and currents.



Assume that **both** D1 and D2 are **cut off**:

In that case, $I_{10k\Omega} = 0 \Rightarrow V_1 = 5 \text{ V}$! Also, $V_2 = 5 - (-5) = 10 \text{ V}$!

but both V_1 and V_2 must be $< 0 \Rightarrow$ our assumption is incorrect.

Assume that **both** D1 and D2 are **turned on**:

In that case, $I_{10k\Omega} = \frac{(5-0)}{(10 \text{ k})} = 0.5 \text{ mA}$. $I_2 = \frac{(0-(-5))}{(5 \text{ k})} = 1 \text{ mA} \Rightarrow I_1 = I_{10k\Omega} - I_2 = -0.5 \text{ mA}$!

$\therefore I_1 < 0$ which contradicts the condition of a turned-on diode $\Rightarrow$ our assumption is incorrect.

Assume that D1 is **on** and D2 is **off**:

In that case, $I_{10k\Omega} = I_1 = \frac{(5-0)}{(10 \text{ k})} = 0.5 \text{ mA}$. $V_2 = 0 - (-5) = 5 \text{ V}$!

$\therefore V_2 > 0 \Rightarrow$ our assumption is incorrect.

Assume that D1 is **off** and D2 is **on**:

In that case, $I_{10k\Omega} = I_2 = \frac{(5-(-5))}{(15 \text{ k})} = (2/3) \text{ mA}$. $V_1 = [5 - (10 \text{ k}) \times (2/3 \text{ mA})] - 0 = -1.667 \text{ V}$ ✓

$\therefore V_1 < 0$ and $I_2 > 0$ that confirms our assumption. 😊

$$\Rightarrow I = I_1 = 0; \text{ and } V = V_1 = (5 \text{ k}) \times (2/3 \text{ mA}) + (-5) = -1.667 \text{ V}$$

Let us resolve the above problem using a constant voltage drop model with $V_D = 0.7$ V;

Assume that **both** D1 and D2 are **cut off**:

In that case, $I_{10k\Omega} = 0 \Rightarrow V_1 = 5$ V ! Also, $V_2 = 5 - (-5) = 10$ V !

$\Rightarrow$ our assumption is incorrect.

Assume that **both** D1 and D2 are turned **on**:

In that case, $I_{10k\Omega} = \frac{(5 - 0.7)}{10 \text{ k}} = 0.43$ mA. $I_2 = \frac{(0.7 - 0.7 - (-5))}{5 \text{ k}} = 1.0$ mA $\Rightarrow I_1 = I_{10k\Omega} - I_2 = -0.57$ mA !

$\because I_1 < 0 \Rightarrow$ our assumption is incorrect.

Assume that D1 is **on** and D2 is **off**:

In that case, $I_{10k\Omega} = I_1 = \frac{5 - 0.7}{10 \text{ k}} = 0.43$ mA. $V_2 = 0.7 - (-5) = 5.7$ V !

$\because V_2 > 0.7 \Rightarrow$ our assumption is incorrect.


Assume that D1 is **off** and D2 is **on**:

In that case, $I_{10k\Omega} = I_2 = \frac{(5 - 0.7 - (-5))}{15 \text{ k}} = 0.62$ mA. $V_1 = [5 - (10 \text{ k}) \times (0.62 \text{ mA})] - 0 = -1.2$ V ✓

$\because V_1 < 0.7$ and $I_2 > 0$ that confirms our assumption. 😊

$$\Rightarrow I = I_1 = 0; \text{ and } V = (5 \text{ k}) \times (0.62 \text{ mA}) + (-5) = -1.9 \text{ V}$$

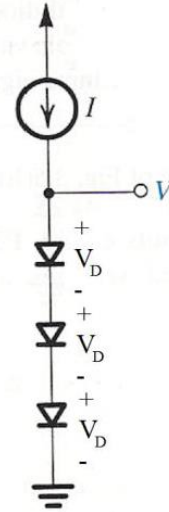3.23 The circuit in Fig. P3.23 utilizes three identical diodes having $n = 1$ and $I_S = 10^{-14}$ A. Find the value of the current I required to obtain an output voltage $V_O = 2$ V. If a current of 1 mA is drawn away from the output terminal by a load, what is the change in output voltage?



∴ the three diodes are identical and conduct the same current (I),

The voltage drop across each diode will be the same $= V_D$.

Now we have $3V_D = 2 \Rightarrow V_D \approx 0.667$ V or 667 mV.

$$\Rightarrow I = 1 \times 10^{-14} \times e^{\frac{667}{1 \times 25.8}} \approx 1.69 \text{ mA}$$


If a current of 1 mA is drawn away from the output terminal that leaves the diodes with 0.69 mA.

The change in a single diode voltage will be $\Delta V_D = 2.3 \times n \times V_T \times \log \frac{0.69}{1.69} = -23.34 \text{ mV}$

$$\Rightarrow \Delta V = 3 \Delta V_D = -70 \text{ mV}$$

i.e., $V_{\text{loaded}} = V + \Delta V = 1930 \text{ mV} = 1.93 \text{ V}$.

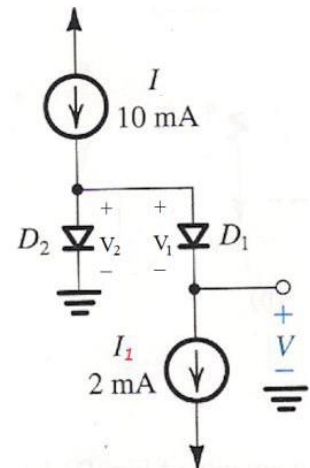3.25 In the circuit shown in Fig. P3.25, both diodes have $n = 1$, but D_1 has 10 times the junction area of D_2 . What value of V results? To obtain a value for V of 50 mV, what current I_1 is needed?



In general,

$$\frac{I_2}{I_1} = \frac{I_{S2}}{I_{S1}} e^{\frac{(V_2 - V_1)}{nV_T}}$$

$$V_2 - V_1 = nV_T \ln\left(\frac{I_2}{I_1} \times \frac{I_{S1}}{I_{S2}}\right)$$

$$V_2 - V_1 = 2.3nV_T \log\left(\frac{I_2}{I_1} \times \frac{I_{S1}}{I_{S2}}\right)$$

For this particular problem, $A_{D1} = 10 A_{D2} \Rightarrow I_{S1} = 10 I_{S2} \Rightarrow \frac{I_{S1}}{I_{S2}} = 10$

Also by inspection $I_2 = I - I_1 = 8 \text{ mA}$.

Writing a node equation starting from the cathode of D_2 and going clockwise,

$$V_2 - V_1 - V = 0 \Rightarrow V = V_2 - V_1 = 60 \times \log\left(\frac{8}{2} \times 10\right) \text{ mV} = 96 \text{ mV}.$$

$$50 = 60 \times \log\left(\frac{10 - I_1}{I_1} \times 10\right) \Rightarrow \log\left(\frac{10 - I_1}{I_1} \times 10\right) = 0.8334 \Rightarrow 10^{0.8334} = \frac{100}{I_1} - 10 \Rightarrow \frac{100}{I_1} = 17.814$$

$$\Rightarrow I_1 = 5.61 \text{ mA}$$

3.27 Several diodes having a range of sizes, but all with $n = 1$, are measured at various temperatures and junction currents as noted below. For each, estimate the diode voltage at 1 mA and 25°C.

- (a) 620 mV at 10 μ A and 0°C
- (b) 790 mV at 1 A and 50°C
- (c) 590 mV at 100 μ A and 100°C
- (d) 850 mV at 10 mA and –50°C
- (e) 700 mV at 100 mA and 75°C

a)

$$V|_{T=25^\circ\text{C}, I=10\mu\text{A}} = V|_{T=0^\circ\text{C}, I=10\mu\text{A}} + (25 - 0) \times (-2 \text{ mV})$$

$$V|_{T=25^\circ\text{C}, I=10\mu\text{A}} = 620 \text{ mV} + (-50 \text{ mV})$$

$$V|_{T=25^\circ\text{C}, I=10\mu\text{A}} = 570 \text{ mV}$$

$$V|_{T=25^\circ\text{C}, I=1\text{mA}} = V|_{T=25^\circ\text{C}, I=10\mu\text{A}} + 2.3nV_T \log\left(\frac{1 \times 10^{-3}}{10 \times 10^{-6}}\right)$$

$$V|_{T=25^\circ\text{C}, I=1\text{mA}} = (570 + 120) \text{ mV} = \mathbf{690 \text{ mV} \Leftarrow}$$

b)

$$V|_{T=25^\circ\text{C}, I=1\text{A}} = V|_{T=50^\circ\text{C}, I=1\text{A}} + (25 - 50) \times (-2 \text{ mV})$$

$$V|_{T=25^\circ\text{C}, I=1\text{A}} = 790 \text{ mV} + 50 \text{ mV}$$

$$V|_{T=25^\circ\text{C}, I=1\text{A}} = 830 \text{ mV} \quad \text{because the current is very large!}$$

$$V|_{T=25^\circ\text{C}, I=1\text{mA}} = V|_{T=25^\circ\text{C}, I=1\text{A}} + 2.3nV_T \log\left(\frac{1 \times 10^{-3}}{1}\right)$$

$$V|_{T=25^\circ\text{C}, I=1\text{mA}} = (830 - 180) \text{ mV} = \mathbf{650 \text{ mV} \Leftarrow}$$

3.34 A “1-mA diode” (i.e., one that has $v_D = 0.7$ V at $i_D = 1$ mA) is connected in series with a $200\text{-}\Omega$ resistor to a 1.0-V supply.

(a) Provide a rough estimate of the diode current you would expect.

(b) If the diode is characterized by $n = 2$, estimate the diode current more closely using iterative analysis.

a)

$$I_2 = \frac{V_s - V_1}{R} = \frac{1 - 0.7}{200} = 1.5 \text{ mA}$$

b)

$$V_2 = V_1 + 2.3nV_T \log\left(\frac{I_2}{I_1}\right) = 0.7 + 0.119 \times \log\left(\frac{1.5}{1}\right) = 0.72095$$

$$I_3 = \frac{V_s - V_2}{R} = \frac{1 - 0.72095}{200} = 1.39525 \text{ mA}$$

$$V_3 = V_2 + 2.3nV_T \log\left(\frac{I_3}{I_2}\right) = 0.72095 + 0.119 \times \log\left(\frac{1.39525}{1.5}\right) = 0.71721$$

$$I_4 = \frac{V_s - V_3}{R} = \frac{1 - 0.71721}{200} = \mathbf{1.41395 \text{ mA}}$$

$$V_4 = V_3 + 2.3nV_T \log\left(\frac{I_4}{I_3}\right) = 0.71721 + 0.119 \times \log\left(\frac{1.41395}{1.39525}\right) = 0.71789$$

$$I_5 = \frac{V_s - V_4}{R} = \frac{1 - 0.71789}{200} = \mathbf{1.41055 \text{ mA}}$$


3.37 Find the parameters of a piecewise-linear model of a diode for which $v_D = 0.7$ V at $i_D = 1$ mA and $n = 2$. The model is to fit exactly at 1 mA and 10 mA. Calculate the error in millivolts in predicting v_D using the piecewise-linear model at $i_D = 0.5$, 5, and 14 mA.

$$\left| \frac{\Delta V_D}{\text{decade}(\Delta I_D)} \right| = 2.3nV_T$$

$$\left| \frac{\Delta V_D}{\text{decade}(\Delta I_D)} \right| = 0.12 \text{ V/decade @ RT for } n = 2$$

I_D (mA)	V_D (V)
1	0.7
10	$0.7 + 0.12 = 0.82$
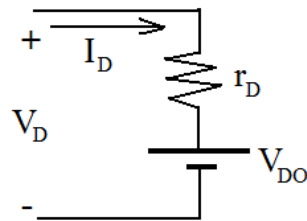
$$r_D = \frac{\Delta V_D}{\Delta I_D} = \frac{0.12}{(10-1) \times 10^{-3}} = 13.34 \, \Omega$$



$$V_D = I_D \times r_D + V_{DO} \Rightarrow V_{DO} = V_D - I_D \times r_D$$

$$V_{DO} = 0.7 - 1 \times 10^{-3} \times 13.34 = 0.687 \text{ V}$$

To calculate V_D exactly, we need to find I_S :



$$I_S = I_D \times e^{-\left(\frac{V_D}{nV_T}\right)} = 1 \times 10^{-3} \times e^{-\left(\frac{0.7}{2 \times 0.0258}\right)} = 1.2835 \times 10^{-9} \text{ A}$$

I_D (mA)	$V_D = nV_T \times \ln\left(\frac{I}{I_S} + 1\right)$	V_D using Piecewise-linear model	Difference (mV)
0.5	0.6642	0.6937	29.5
5	0.7831	0.7537	-29.4
14	0.8362	0.8738	37.6

Graphical Analysis (Load Line Method):

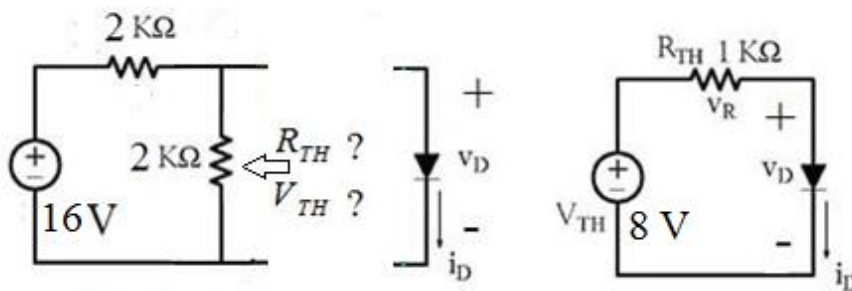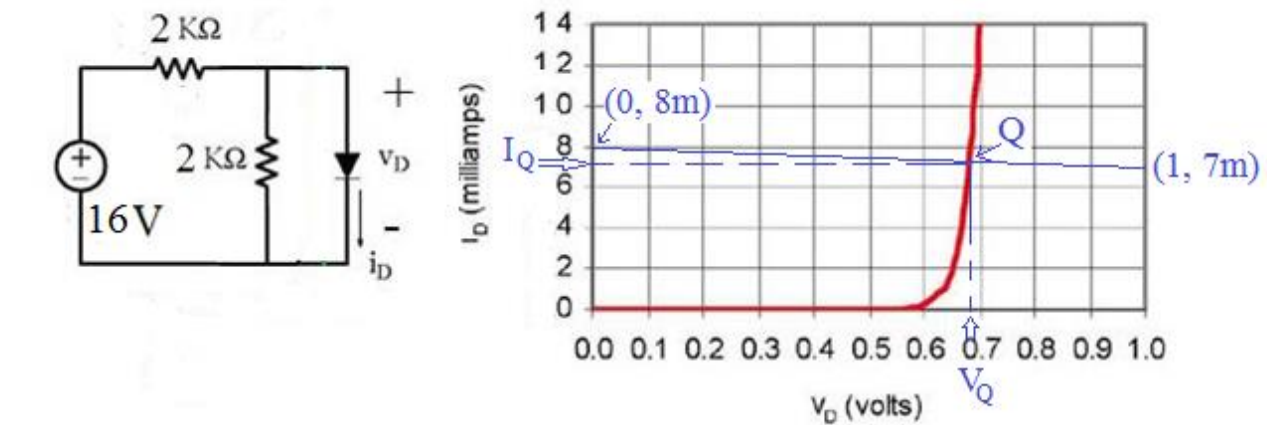- Example 1:

The diode used in the circuit below has the i-v characteristic shown to the right. Find the the dc operating (bias) point Q.



Load Line Equation

$$V_{TH} = I_D \times R_{TH} + V_D$$

$$8 = I_D \times 1000 + V_D$$


$$@V_D = 0 \text{ V} \rightarrow I_D = 8 \text{ mA}$$

$$@V_D = 1 \text{ V} \rightarrow I_D = 7 \text{ mA}$$

- Example 2


In the given i-v characteristic below, which load line represent the given circuit?

Answer: Number 2.

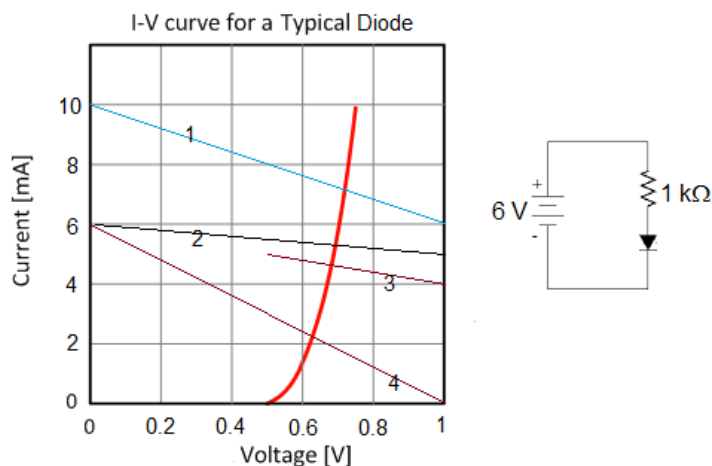


3.56 In the capacitor-coupled attenuator circuit shown in Fig. P3.56, I is a dc current that varies from 0 mA to 1 mA, D_1 and D_2 are diodes with $n = 1$, and C_1 and C_2 are large coupling capacitors. For very small input signals, find the values of the ratio v_o/v_i for I equal to:

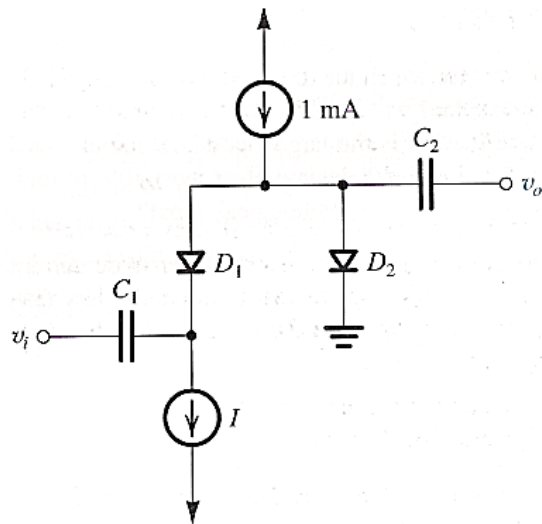- (a) 0 μ A
- (b) 1 μ A
- (c) 10 μ A
- (d) 100 μ A
- (e) 500 μ A
- (f) 600 μ A
- (g) 900 μ A
- (h) 990 μ A
- (i) 1 mA



d) $I = 100 \mu$ A


DC Equivalent circuit:

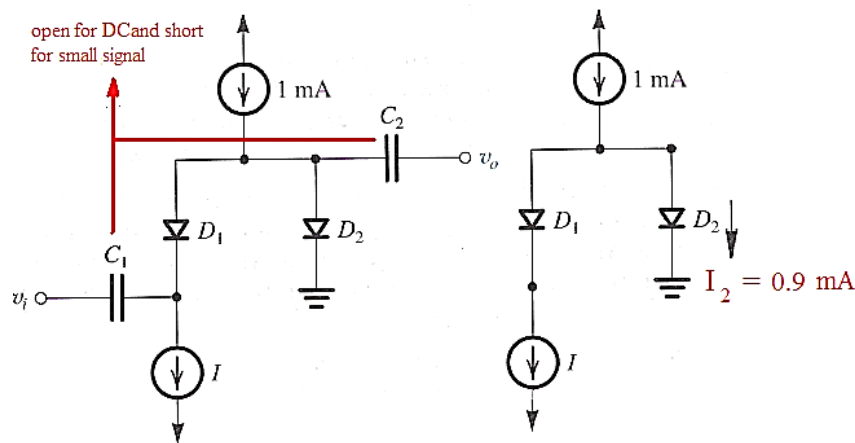

Small Signal Equivalent circuit:

$$r_{d1} = \frac{nV_T}{I_1} = \frac{1 \times 0.0259}{100 \times 10^{-6}} = 259 \Omega$$
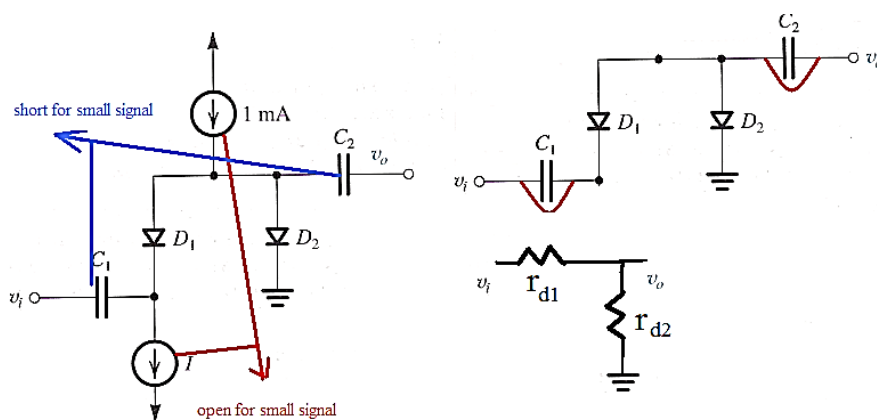
$$r_{d2} = \frac{nV_T}{I_2} = \frac{1 \times 0.0259}{0.9 \times 10^{-3}} = 28.78 \Omega$$



$$\frac{v_o}{v_i} = \frac{r_{d2}}{r_{d2} + r_{d1}} = \frac{28.78}{28.78 + 259} = 0.1 \text{ V/V}$$

3.107)

A young designer, aiming to develop intuition, concerning conducting paths within an integrated circuit, examines the end-to-end resistance of a connecting bar 10 μm long, 3 μm wide, 1 μm thick, made of various materials. The designer considers:

- intrinsic silicon
- n -doped silicon with $N_D = 1 \times 10^{16}/\text{cm}^3$
- n -doped silicon with $N_D = 1 \times 10^{18}/\text{cm}^3$
- p -doped silicon with $N_D = 1 \times 10^{10}/\text{cm}^3$
- aluminum with resistivity of $2.8 \mu\Omega\cdot\text{cm}$

Find the resistance in each case. For intrinsic silicon, use $\mu_n = 1350 \text{ cm}^2/\text{V}\cdot\text{s}$, $\mu_p = 480 \text{ cm}^2/\text{V}\cdot\text{s}$, and $n_i = 1.5 \times 10^{10}/\text{cm}^3$. For doped silicon, assume $\mu_n \cong 2.5\mu_p = 1200 \text{ cm}^2/\text{V}\cdot\text{s}$. (Recall that $R = \rho L/A$.)

In general,

$$n = \frac{N_D - N_A}{2} + \sqrt{\left(\frac{N_D - N_A}{2}\right)^2 + n_i^2} \quad ; \text{and} \quad p = \frac{N_A - N_D}{2} + \sqrt{\left(\frac{N_A - N_D}{2}\right)^2 + n_i^2}$$

$$a) \quad n = p = n_i \Rightarrow R = \frac{\rho L}{A} = \frac{L}{\sigma A} = \frac{L}{[q(n\mu_n + p\mu_p)]A} = \frac{L}{[qn_i(\mu_n + \mu_p)]A} \Rightarrow$$

$$R = \frac{10 \times 10^{-4}}{1.602 \times 10^{-19} \times 1.5 \times 10^{10} (1350 + 480) \times 3 \times 10^{-4} \times 1 \times 10^{-4}} = 7.58 \times 10^9 \Omega = 7.59 \text{ G}\Omega$$

$$b) \quad n = N_D; p = \frac{n_i^2}{N_D} \Rightarrow R = \frac{\rho L}{A} = \frac{L}{\sigma A} = \frac{L}{q \left(N_D \mu_n + \frac{n_i^2}{N_D} \mu_p \right) A} \approx \frac{L}{q(N_D \mu_n)A}$$

$$(\text{note: } N_D \mu_n \gg \frac{n_i^2}{N_D} \mu_p) \Rightarrow$$

$$R = \frac{10 \times 10^{-4}}{1.602 \times 10^{-19} \times 1 \times 10^{16} \times 1200 \times 3 \times 10^{-4} \times 1 \times 10^{-4}} = 17361 \Omega = 17.361 \text{ k}\Omega$$

d) Since N_A is comparable to n_i ,

$$p = \frac{N_A - N_D}{2} + \sqrt{\left(\frac{N_A - N_D}{2}\right)^2 + n_i^2} = 2.08 \times 10^{10} \text{ cm}^{-3}; \quad n = \frac{n_i^2}{p} = 1.08 \times 10^{10} \text{ cm}^{-3}$$

$$R = \frac{\rho L}{A} = \frac{L}{\sigma A} = \frac{L}{q(n\mu_n + p\mu_p)A}$$

$$R = \frac{10 \times 10^{-4}}{1.602 \times 10^{-19}(2.08 \times 10^{10} \times 480 + 1.08 \times 10^{10} \times 1200) \times 3 \times 10^{-4} \times 1 \times 10^{-4}} = 9.07 \text{ G}\Omega$$

$$e) R = \frac{\rho L}{A} = \frac{2.8 \times 10^{-6} \times 10 \times 10^{-4}}{3 \times 10^{-4} \times 1 \times 10^{-4}} = 0.0934 \text{ } \Omega = 93.4 \text{ m}\Omega$$

3.108)

Holes are being steadily injected into a region of n-type silicon. In the Steady state, the excess-hole concentration profile shown in Fig P3.108 Is established in the n-type silicon region. Here “excess” means over and above the concentration p_{no} .

If $N_D = 10^{16} / \text{cm}^3$, $n_i = 1.5 \times 10^{10} / \text{cm}^3$ and $W = 5 \mu\text{m}$, find the density of the current that will flow in the x direction.

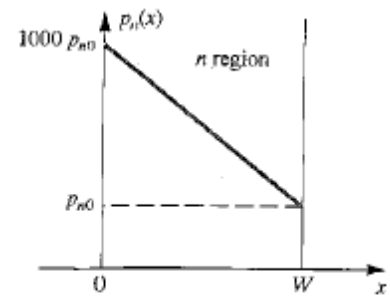


FIGURE P3.108

$$J_p = -qD_p \frac{dp}{dx}$$


$$p_{no} = \frac{n_i^2}{n_{no}} = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10})^2}{10^{16}} = 2.25 \times 10^4 \text{ cm}^{-3}$$

$$\frac{dp}{dx} = \frac{p_{no} - 1000p_{no}}{W - 0} = \frac{-999p_{no}}{W} = \frac{-999 \times 2.25 \times 10^4}{5 \times 10^{-4}} = -4.4955 \times 10^{10} \text{ cm}^{-4}$$

$$J_p = -qD_p \frac{dp}{dx} = -1.602 \times 10^{-19} \times 12 \times (-4.4955 \times 10^{10}) = 8.64 \times 10^{-8} \text{ A/cm}^2$$

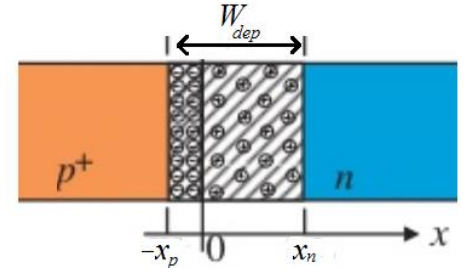3.115)

If for a particular junction, the acceptor concentration is $1 \times 10^{16}/\text{cm}^3$ and the donor concentration is $1 \times 10^{15}/\text{cm}^3$, find the junction built-in voltage (barrier voltage). Assume $n_i = 1 \times 10^{10}/\text{cm}^3$. Also, find W_{dep} and its extent in each of the p and n regions when the junction is reverse biased with $V_R = 5 \text{ V}$. At this value of the reverse bias, calculate the magnitude of the charge stored on either side of the junction.



Assume the junction area is $400 \mu\text{m}^2$. Also, calculate C_j .

$$V_O = V_T \times \ln \frac{N_A \times N_D}{n_i^2}$$

$$V_O = 0.0258 \times \ln \frac{10^{16} \times 10^{15}}{(10^{10})^2}$$

$$V_O = 0.653 \text{ V}$$

$$W_{dep} = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_O + V_R)}$$

$$W_{dep} = \sqrt{\frac{2 \times 11.7 \times 8.854 \times 10^{-14}}{1.602 \times 10^{-19}} \left(\frac{1}{10^{16}} + \frac{1}{10^{15}} \right) (0.653 + 5)} = 2.836 \times 10^{-4} \text{ cm} = 2.836 \mu\text{m}$$

$$W_{dep} = x_p + x_n \rightarrow x_p + x_n = 2.836 \quad \text{①} \quad ; \quad \frac{x_p}{x_n} = \frac{N_D}{N_A} \rightarrow \frac{x_p}{x_n} = \frac{10^{15}}{10^{16}} \rightarrow \frac{x_n}{x_p} = 10 \quad \text{②}$$

Solving ① and ② simultaneously yields:

$$x_p = \frac{2.836}{11} = 0.258 \mu\text{m} \quad \text{and} \quad x_n = 2.578 \mu\text{m}$$

$$q_j = qN_D x_n A = qN_A x_p A = 1.602 \times 10^{-19} \times 10^{16} \times 0.2578 \times 10^{-4} \times 400 \times 10^{-8} = 1.652 \times 10^{-13} \text{ C}$$

$$C_j = \frac{\epsilon_s \times A}{W_{dep}} = \frac{11.7 \times 8.854 \times 10^{-14} \times 400 \times 10^{-8}}{2.836 \times 10^{-4}} = 1.461 \times 10^{-14} \text{ F} = 14.61 \text{ fF}$$

3.121)

A p^+-n diode is one in which the doping concentration in the p region is much greater than that in the n region. In such a diode, the forward current is mostly due to the hole injection across the junction. Show that:

$$I \approx I_p = Aqn_i^2 \left(\frac{D_p}{L_p N_D} \right) \left(e^{\frac{V}{V_T}} - 1 \right)$$

For the specific case in which $N_D = 5 \times 10^{16}/\text{cm}^3$, $D_p = 10 \text{ cm}^2/\text{s}$, $\tau_p = 0.1 \mu\text{s}$, and $A = 10^4 \mu\text{m}^2$, find I_S and the voltage V obtained when $I = 0.2 \text{ mA}$. Assume operation at 300 K where $n_i = 1.5 \times 10^{10}/\text{cm}^3$. Also, calculate the excess minority-carrier charge and the value of the diffusion capacitance at $I = 0.2 \text{ mA}$.

$$I = I_S \left(e^{\frac{V}{V_T}} - 1 \right) = I_p + I_n$$

$$\text{Where } I_S = Aqn_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) \Rightarrow I = Aqn_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) \left(e^{\frac{V}{V_T}} - 1 \right)$$

$$I_p = Aqn_i^2 \left(\frac{D_p}{L_p N_D} \right) \left(e^{\frac{V}{V_T}} - 1 \right) \text{ and } I_n = Aqn_i^2 \left(\frac{D_n}{L_n N_A} \right) \left(e^{\frac{V}{V_T}} - 1 \right)$$

$$\because \text{the junction is } p^+-n \Rightarrow N_A \gg N_D \Rightarrow I_p \gg I_n \Rightarrow I \approx I_p$$

$$I_p = Aqn_i^2 \left(\frac{D_p}{L_p N_D} \right) \left(e^{\frac{V}{V_T}} - 1 \right) \approx I = 0.2 \text{ mA}$$

$$L_p = \sqrt{D_p \tau_p} = \sqrt{10 \times 0.1 \times 10^{-6}} = 1 \times 10^{-3} \text{ cm}$$

$$I_S \approx Aqn_i^2 \left(\frac{D_p}{L_p N_D} \right) = 10^4 \times 10^{-8} \times 1.602^{-19} \times (1.5 \times 10^{10})^2 \frac{10}{1 \times 10^{-3} \times 5 \times 10^{16}} = 0.72 \times 10^{-15} \text{ A}$$

$$V \approx V_T \ln \left(\frac{I_p}{I_S} + 1 \right) = 0.0258 \times 26.35 = 0.6798 \text{ V}$$

$$Q_p = \tau_p I_p = 0.1 \times 10^{-6} \times 0.2 \times 10^{-3} = 2 \times 10^{-11} \text{ C} = 20 \text{ pC}$$

$$C_d = \frac{Q}{V_T} = \frac{Q_p + Q_n}{V_T} \approx \frac{Q_p}{V_T} = \frac{\tau_p I_p}{V_T} = 7.752 \times 10^{-10} = 0.7752 \text{ nF}$$